


Computer Architecture Final Project

B04502040 徐瑞擇 B05901182 潘彥銘 B05901062 阮明皓

Briefly describe your CPU architecture

The CPU architecture has 2 parts: Combinational part and sequential part.

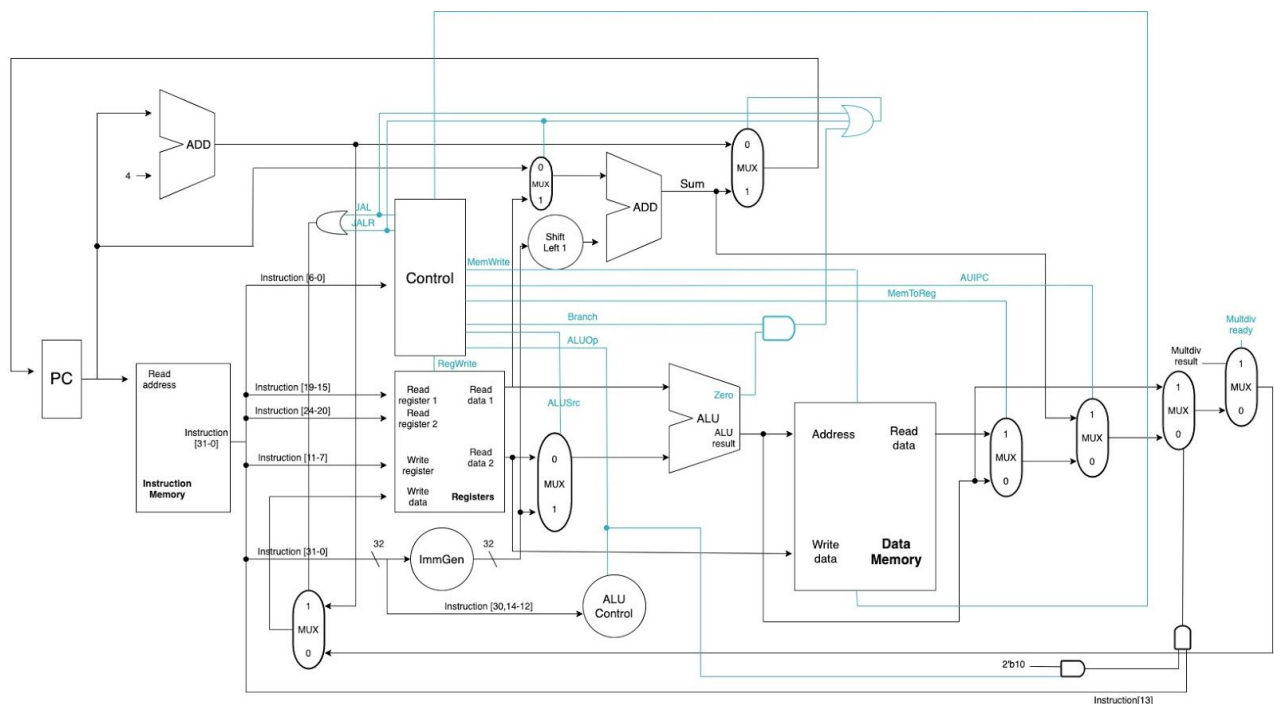Combinational part (Part other than multiplication and division):



The Control lines are shown as above. First, we added JAL, JALR and AUIPC outputs to the Control module. Whenever a JAL/JALR/AUIPC instruction is detected, the line corresponding will turn up and send out control signals.

To determine which data should be written back to the register file, we added several MUXs in sequence. The code looks like this:

```
// where does the data to be stored in register come from?
assign m1 = (MemToReg)? mem_rdata_D:ALU_result; // from alu result or data memory
assign m2 = (AUIPC)? Sum:m1;
assign m3 = (ALUOp == 2'b10 && Instruction[13])? ALU_result[31] : m2; // slti
assign m4 = (multDiv_ready)? multDiv_result : m3; // mul
assign rd_data = (JAL || JALR)? PC+4:m4;
```

To determine the next address PC points to, we need to know whether the instruction is JAL or JALR.

```
assign Add1 = (JALR)?rs1_data:PC;
assign Sum = (JALR||JAL)?Add1 + ImmGen_out:Add1 + (ImmGen_out << 1);
```

The next PC is then chosen between Sum and PC+4 based on JAL, JALR, Branch and ALU_Zero signals:

```
always @(*) begin
    if (!MULT_mode_nxt) begin
        if (JAL || JALR || (Branch && ALU_Zero)) begin
            PC_nxt_w = Sum;
        end
        else begin
            PC_nxt_w = PC + 4;
        end
    end
    else begin
        PC_nxt_w = PC;
    end
end
```


Control:

Instruction	AluSrc	Memto-Reg	Reg-Write	Mem-Read	Mem-Write	Branch	ALUOp1	ALUOp0	JAL	JALR	AUIPC
Add/Sub	0	0	1	0	0	0	1	0	0	0	0
addi/slti	1	0	1	0	0	0	1	0	0	0	0
lw	1	1	1	1	0	0	0	0	0	0	0
sw	1	x	0	0	1	0	0	0	0	0	0
beq	0	x	0	0	0	1	0	1	0	0	0
jal	x	x	1	0	0	0	x	x	1	0	0
jalr	x	x	1	0	0	0	x	x	0	1	0
auipc	1	x	1	0	0	0	x	x	0	0	1

ALU_Control:

Instruction Opcode	ALUOp	Operation	Funct7 field	Funct3 field	Desired ALU action	ALU control input
lw	00	Load word	x	x	add	0010
sw	00	Store word	x	x	add	0010
beq	01	Branch if equal	x	x	subtract	0110
add	10	add	0000000	000	add	0010
sub	10	sub	0100000	000	subtract	0110
addi	10	add immediate	x	000	add	0010
slti	10	store 1 if less than imm	x	010	subtract	0110
jal	00	Jump and Link	x	x	add	0010
jalr	00	Indirect Jump	x	x	add	0010
auipc	00	Store pc-relative addr	x	x	add	0010
mul	10	multiply	0000001	000	mult	1000

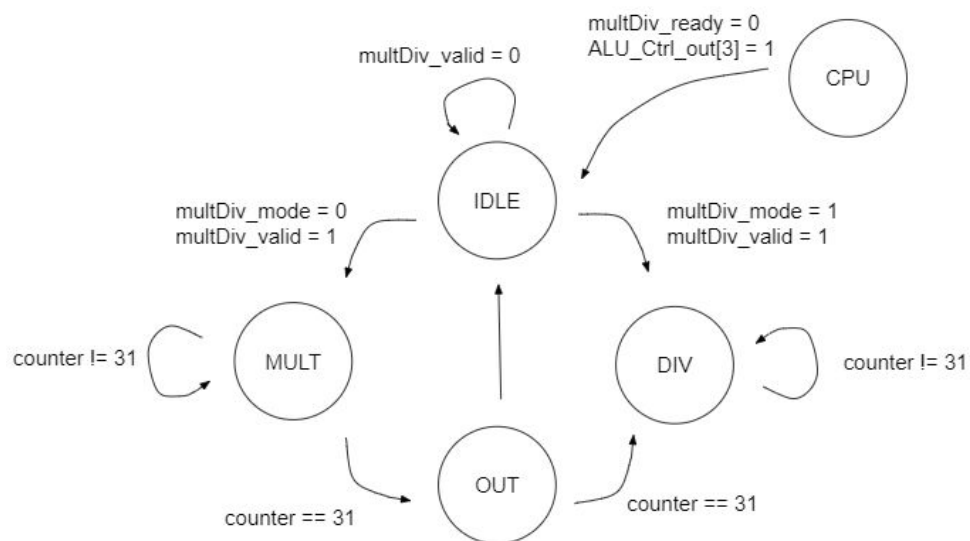Sequential part (FSM for multiplication and division):



We first detect if the ready bit is 0 and the LSB of ALU control output is 1, if both of the conditions above satisfy, then our CPU will do multi-cycle operation, which depends on the mulDiv_mode. If

mulDiv_mode is 0, our CPU will do multiplication. If mulDiv_mode is 1, our CPU will do division. The remaining steps are same as that in HW3.

Record total simulation time (CYCLE = 10 ns)

- Leaf: a = 1, b = 9, c = 2, d = 2

```
Simulation complete via $finish(1) at time 255 NS + 0
```

- Fact: n = 10

```
Simulation complete via $finish(1) at time 4895 NS + 0
```

- (Bonus) HW1: n = 10

```
Simulation complete via $finish(1) at time 3735 NS + 0
```

Describe your observation

At first we did not design our control classification properly. Therefore, we have to additionally add a few MUXs to implement the functions, which increases the datapath.

Also, for bonus, we have to adjust the data size and the stack size so that the program can execute seamlessly.

Snapshot the “Register table” in Design Compiler (p. 22)

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
alu_in_reg	Flip-flop	32	Y	N	Y	N	N	N	N
ready_reg_reg	Flip-flop	1	N	N	Y	N	N	N	N
counter_reg	Flip-flop	5	Y	N	Y	N	N	N	N
state_reg	Flip-flop	2	Y	N	Y	N	N	N	N
shreg_reg	Flip-flop	64	Y	N	Y	N	N	N	N

List a work distribution table

	徐瑞擇	阮明皓	潘彥銘
工作分配	想架構、接上大家的module、寫report	接上MUL、做bonus	寫code、寫report

